

## 2. BOOLEAN ALGEBRA (or) SWITCHING ALGEBRA 16

Boolean algebra is used to simplify boolean equations, to make simple logic circuits.

Representation of Boolean function (or) switching function

(or) logical function :-

Ex:-  $Y = ab + bc$

→  $a, b, c$  are called variables (or) literals, which are inputs for the logic gates.

→ To implement a logic function with less no. of gates we have to minimise variables & the number of terms.

Boolean algebra rules :-

(i) commutative law

$$A + B = B + A$$

$$A \cdot B = B \cdot A$$

(ii) Associative law

$$A + (B + C) = (A + B) + C$$

$$(AB)C = A(BC)$$

(iii) Distributive law

$$A(B + C) = AB + AC$$

$$A + BC = (A + B)(A + C)$$

(iv) Additive law

$$A + 0 = A$$

$$A + A = A$$

$$A + 1 = 1$$

$$A + \bar{A} = 1$$

(v) multiplication property.

$$A \cdot 0 = 0$$

$$A \cdot 1 = A$$

$$A \cdot A = A$$

$$A \cdot \bar{A} = 0$$

(vi) Double negation.

$$\overline{(\bar{A})} = A$$

(vii) Absorption law

$$A(A+B) = A$$

$$A + AB = A$$

$$A(\bar{A}+B) = AB$$

$$AB + \bar{B} = A + \bar{B}$$

$$A\bar{B} + B = A + B$$

(viii) Duality property.  $AB + \bar{A}\bar{B} = (A+B)(\bar{A}+\bar{B})$

(ix) Demorgan's theorem.  $\overline{A \cdot B} = \bar{A} + \bar{B}$

$$\overline{A+B} = \bar{A} \cdot \bar{B}$$

(x) consensus theorem.  $AB + \bar{A}C + BC = AB + \bar{A}C$

① Prove that  $(A+B)(A+C) = A+BC$ .

Proof:- L.H.S =  $(A+B)(A+C)$

$$= AA + AC + BA + BC \quad (\because AA = A)$$

$$= A + AC + BA + BC$$

$$= BC + (1+C+B)A \quad (\because 1+A=1)$$

$$= A + BC$$

$$= \text{R.H.S.}$$

(1 + Anything = 1 in logical gates).

$$\therefore \boxed{A+BC = (A+B)(A+C)}$$

Ex:- Simplify following boolean expressions to a min. (17)  
no. of variables or literals. ( $\bar{B}$  or  $B'$  both are same)

Q ①  $(A+B)(A+\bar{B})$

Sol:-  $(A+B)(A+\bar{B}) = A \cdot A + A \cdot \bar{B} + B \cdot A + B \cdot \bar{B}$   
 $= A + A \cdot \bar{B} + B \cdot A + 0$   
 $= A(1 + B + \bar{B})$   
 $= A(1 + 1)$  ( $\because 1 + \text{anything} = 1$ )  
 $= A$

②  $xy + xyz + xy\bar{z} + \bar{x}yz$

Sol:-  $xy + xyz + xy\bar{z} + \bar{x}yz$   
 $= xy[1 + z + \bar{z}] + \bar{x}yz$  ( $\because 1 + \text{anything} = 1$ )  
 $= xy \cdot 1 + \bar{x}yz$   
 $= \bar{x}yz + xy$  ( $\because A + BC = (A+B)(A+C)$ )  
 $= y[\bar{x}z + x] = y[(x + \bar{x}) + (x + z)]$   
 $= xy[x + z]$

23/07/2014  
③  $x'y + xy' + xy + x'y'$

Sol:-  $x'[y + y'] + x[y + y']$   
 $= x'[1] + x[1] = x + x' = 1$

④  $\bar{A} + AB + A\bar{C} + A\bar{B}\bar{C}$

Sol:-  $\bar{A} + AB + A\bar{C}(A + A\bar{B})$  |  $\bar{A} + AB + A\bar{C}(1 + \bar{B})$   
 $= \bar{A} + AB + A\bar{C}(1)$  |  $= \bar{A} + AB + A\bar{C}$   
 $= \bar{A} + A(B + \bar{C})$  |  $= (A + \bar{A})(\bar{A} + B) + A\bar{C}$   
 $= 1 - A + AB + A\bar{C}(1 - C)$  |  $= \bar{A} + B + A\bar{C}$  ( $\because$  distributive law)  
 $= 1 - A\bar{C}$  |  $= \bar{A} + A\bar{C} + B$   
 $= 1 - A + AB + A - AC$  |  $= (\bar{A} + A)(\bar{A} + \bar{C}) + B$   
 $= 1 - A\bar{C}$  |  $= \bar{A} + \bar{C} + B$



⑤  $ABC + \bar{A}B + AB\bar{C}$

Sol:-  $ABC + AB\bar{C} + \bar{A}B$   
 $= AB(C + \bar{C}) + \bar{A}B$   
 $= AB + \bar{A}B$   
 $= B(A + \bar{A}) = B$

⑥  $x'y' + xy + x'y$

Sol:-  $x'(y' + y) + xy$   
 $= x' + xy$   
 $= (x' + x)(x' + y) \quad (\because \text{distributive law})$   
 $= x' + y$

⑦  $a + a'b + a'b'c + a'b'c'd + \dots$

Sol:-  $a + a'[b + b'c + b'c'd + \dots]$  (absorption law)  
 $\therefore A + \bar{A}B = A + B$   
 $= a + b + b'c + b'c'd + \dots$   
 $= a + b + b'[c + c'd + c'd'e + \dots]$  ( $\because$  absorption law)  
 $A + \bar{A}B = A + B$   
 $= a + b + c + c'd + c'd'e + \dots$   
 $\vdots$   
 $= a + b + c + d + e + \dots$

⑧ prove that  $A(\bar{A} + c)(\bar{A}B + \bar{c}) = 0$

Sol:-  $(A\bar{A} + AC)(\bar{A}B + \bar{c})$   
 $= AC(\bar{A}B + \bar{c})$   
 $= AC\bar{A}B + AC\bar{c} \quad (\because A\bar{A} = 0)$   
 $= (A\bar{A})BC + A(0)$   
 $= 0 + 0 = 0$

⑨ P.T  $(A+C)(A+D)(B+C)(B+D) = AB+CD$

Sol:-  $[A \cdot A + AD + CA + CD][B \cdot B + BD + CB + CD]$

$= [A + AD + CA + CD][B + BD + CB + CD]$

$(A+C)(A+D)(B+C)(B+D)$

$(\because A+BC = (A+B)(A+C))$

$= (A+CD)(B+CD)$

$= CD + AB$

⑩ P.T  $AB + \bar{A}\bar{C} + A\bar{B}C(AB+C) = 1$

Sol:-  $AB + \bar{A} + \bar{C} + \underbrace{A\bar{B}C \cdot AB}_0 + A\bar{B}C \cdot C$

$\therefore \bar{B} \cdot B = 0$   
 $\therefore AB + \bar{A}\bar{C} + A\bar{B}C$

$= (A+B)(\bar{A}+\bar{C}) + A\bar{B}C$

$= AB + \bar{A}\bar{C} + A\bar{B}C$

$= A(B + \bar{B}C) + \bar{A}\bar{C}$

$(\because A+BC = (A+B)(A+C))$

$= A[(B+\bar{B}) + (B+C)] + \bar{A}\bar{C}$

$(\because B+\bar{B} = 1)$

$= AB + \underbrace{AC + \bar{A}\bar{C}}_1$

$= 1 + AB$

$(\because 1 + \text{anything} = 1)$

$= 1$

⑪ Prove that  $\bar{A}\bar{B}\bar{C} + \bar{A}B\bar{C} + A\bar{B}\bar{C} + A\bar{B}C = \bar{C}$

Sol:-  $\bar{A}\bar{C}[B+\bar{B}] + A\bar{C}[B+\bar{B}]$

$(\because A+\bar{A} = 1)$

$= \bar{A}\bar{C} + A\bar{C}$

$= \bar{C}[A+\bar{A}] = \bar{C}$

Ex:- Reduce the following Boolean expression to indicated no. of variables or literals.

(12)  $\bar{A}\bar{C} + ABC + A\bar{C}$  to 3 literals.

Sol:-  $(\bar{A} + A)\bar{C} + ABC$   
 $= \bar{C} + ABC$   
 $= \bar{C} + C \cdot AB$   $(\because A + BC = (A+B)(A+C))$   
 $= (\bar{C} + C)(\bar{C} + AB)$   $(\bar{A} + A = 1)$   
 $= \bar{C} + AB$

(13)  $(\overline{xy + z}) + z + xy + wz$  to 3 variables.

Sol:-  $(\overline{xy}) + \bar{z} + z + xy + wz$   $(\because \overline{A+B} = \bar{A} \cdot \bar{B})$   
 $xy\bar{z} + z + xy + wz$   
 $= z + \bar{z} \cdot xy + xy + wz$   $(\because A + BC = (A+B)(A+C))$   
 $= (z + \bar{z})(z + xy) + xy + wz$   
 $= z + xy + xy + wz$   
 $= z(1+w) + xy(1+1)$   
 $= z + xy$   
 $= xy(1+\bar{z}) + z(1+w)$   
 $= xy + z$   $(\because 1 + \text{anything} = 1)$

(13) (i)  $(\overline{xy + z}) + z + xy + wz$  to 3 variables.

Sol:-  $\bar{x} \cdot \bar{y} \cdot \bar{z} + z + xy + wz$   
 $(\bar{x} + \bar{y})\bar{z} + z(1+w) + xy$   
 $= xy\bar{z} + xy +$   
 $= x\bar{z} + y\bar{z} + z + xy$   
 $= z + x\bar{z} + y\bar{z} + xy$   
 $= (z+x)(z+\bar{z}) + y\bar{z} + xy$   
 $= z + z + xy + x\bar{z} = x(1+y) + (z+y)(z+\bar{z})$



$$= x + y + z$$

( $\therefore$  1 + anything = 1)

$$A + \bar{A} = 1$$

⑭  $A'B(c'D + D') + B(A + A'CD)$  to 1 literal

Sol:  $A'BC'D + A'BD' + AB + A'BCD$

$$= A'BD(c + c') + AB + A'BD' \quad (\because A + Bc = (A+B)(A+c))$$

$$= A'BD + AB + A'BD' \quad (A + \bar{A} = 1)$$

$$= A'B(D + D') + AB$$

$$= A'B + AB = B(A + A') = \underline{\underline{B}}$$

Ex: Find the complement of the Boolean function and reducing to a minimum number of variables.

Sol: ⑮  $(B\bar{C} + \bar{A}D)(A\bar{B} + C\bar{D})$

Sol: after taking complement

$$\overline{(B\bar{C} + \bar{A}D)(A\bar{B} + C\bar{D})}$$

$$= \overline{(AB\bar{B}\bar{C} + B\bar{C}C\bar{D} + A\bar{A}D\bar{B} + \bar{A}DC\bar{D})} \quad (\because A \cdot \bar{A} = 0)$$

$$= \overline{0} = 1$$

⑯  $x'(y' + z')(x + y + z')$

Sol:  $\overline{x'(y' + z')(x + y + z')}$

$$= \overline{(x'y' + x'z')(x + y + z')}$$

$$= \overline{(x'y'x + x'z'x + x'y'y + x'y'z' + x'z'y + x'z \cdot z')}$$

$$= \overline{x'y'z' + x'z'y + x'z}$$

$$= \overline{x'z'(y + y') + x'z}$$

$$= \overline{x'z' + x'z'} \quad (= \overline{x'(z + z')})$$

$$= \overline{x'z'(1+1)} = \overline{x'z'} = \overline{x'z}$$

$$= \overline{\bar{x}\bar{z}} = xz$$

$$= (\bar{x}) + (\bar{z}) = x + z$$

(17) Find dual of  $F = \bar{A}B + BC + A\bar{C}$

Sol. Duality of  $F = (\bar{A}+B)(B+C)(A+\bar{C})$

Sub.  $x's \rightarrow +s$   
 $+s \rightarrow x's$   
 $0's \rightarrow 1's$   
 $1's \rightarrow 0's$

(18) Find dual of  $xy + x'z = 0$

Sol. Duality  $\Rightarrow (x+y)(x'+z) = 1$

## LOGIC GATES :-

1. Inverter (or) NOT gate :-

'NOT' Gate performs inversion operation.

It has '1' input and one output.

Logic Symbol :-



Truth Table :- Truth table indicates outputs for different possibilities of input.



i/p	o/p
A	$Y = \bar{A}$
0	1
1	0

Timing diagram :-

The input & output wave

forms showing time relationship is called

Timing diagram.

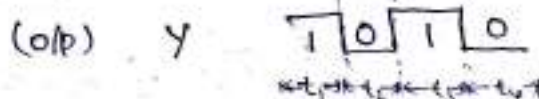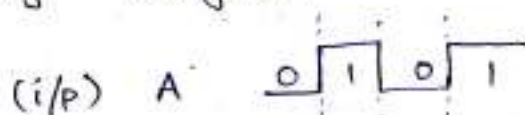



## 2. Buffer gate :-



output is same as the i/p

$$i/p = o/p$$


It is used for time delay.

## 3. AND gate :-

'AND' gate performs logical multiplication.

It has two or more i/p's and one output.


Logic symbol :-

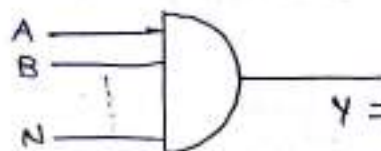

$$\begin{aligned} Y &= A \text{ and } B \text{ and } \dots N \\ &= A \cdot B \cdot \dots N \\ &= AB \dots N \end{aligned}$$

### 2 i/p AND gate :-

Logic symbol :-

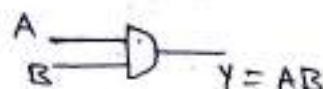


Truth table :-

i/p's		o/p
A	B	Y
0	0	0
0	1	0
1	0	0
1	1	1

AND gate o/p is high when all i/p's are high.

Timing diagram :-

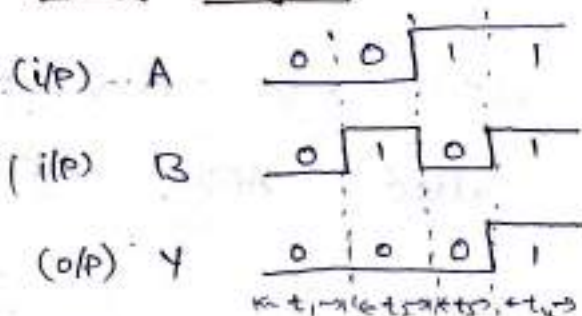

### 1 i/p AND gate :-




#### ④ OR gate :-


(722)

OR gate performs logical Addition. It has two or more inputs & one output.


logic symbol:-

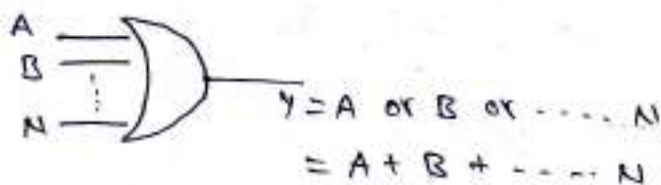

1 i/p OR gate:-

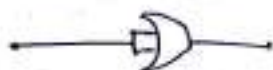

2 i/p OR gate:-

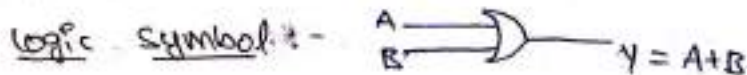


Truth table:-

i/p's		o/p
A	B	y
0	0	0
1	0	1
0	1	1
1	1	1

OR gate o/p is low when all the inputs are low.

Timing diagram:-

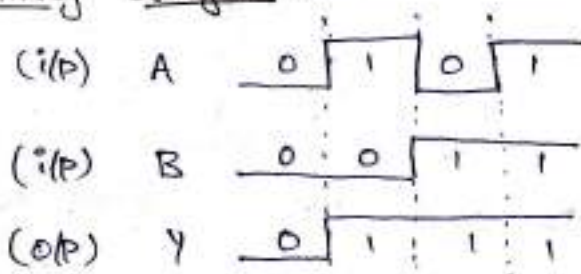


Note:- Logic circuits which use AND, OR, NOT gates only are called AOI logic circuits

## Universal gates :-


NAND & NOR are called universal gates because by using either NAND or NOR gates we can implement any logic circuit.

NAND gate :- The term NAND is a combination of AND & NOT gates.

### logic symbol :-

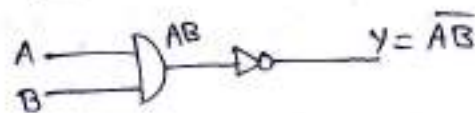

### 2 i/p NAND gate :-

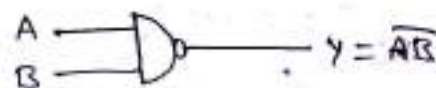


### Truth table :-

i/p's		o/p
A	B	Y
0	0	1
0	1	1
1	0	1
1	1	0

NAND gate o/p is low when the all the i/p's are high.

NOR gate :- The term NOR is a combination of OR & NOT gates.

### logic symbol :-

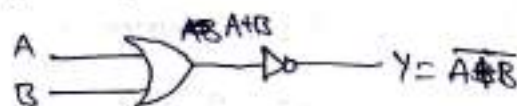

### 2 i/p's NOR gate :-






Truth Table :-

i/p's		o/p
A	B	Y
0	0	1
1	0	0
0	1	0
1	1	0

NOR gate o/p is high when all i/p's are low.

EXOR (or) XOR (or) EXCLUSIVE-OR gate :-

logic symbol :-

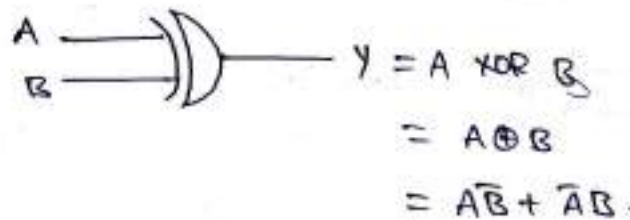


Truth table :-

i/p's		o/p
A	B	Y
0	0	0
0	1	1
1	0	1
1	1	0

XOR o/p is low when all i/p's are same.

EXNOR (or) XNOR (or) EXCLUSIVE NOR gate :-

logic symbol :-

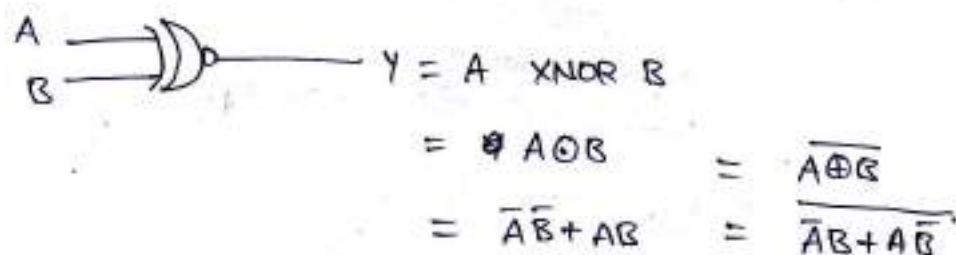

Truth Table:-

i/p's		o/p
A	B	Y
0	0	1
0	1	0
1	0	0
1	1	1

EXNOR o/p is high when all i/p's are same.

Note:- dual of XOR gate is XNOR.



30/07/2014

\* Dual of XOR gate is XNOR.

$$\begin{aligned}
 \text{dual of } \bar{A}B + A\bar{B} &= (\bar{A}+B)(A+\bar{B}) \\
 &= \bar{A} \cdot A + \bar{A} \cdot \bar{B} + B \cdot A + B \cdot \bar{B} \\
 &= \bar{A}\bar{B} + AB
 \end{aligned}$$


Ex:- Implement  $F = \bar{A}B + AB\bar{C} + B\bar{C}$  using basic logic gates.

Sol:-

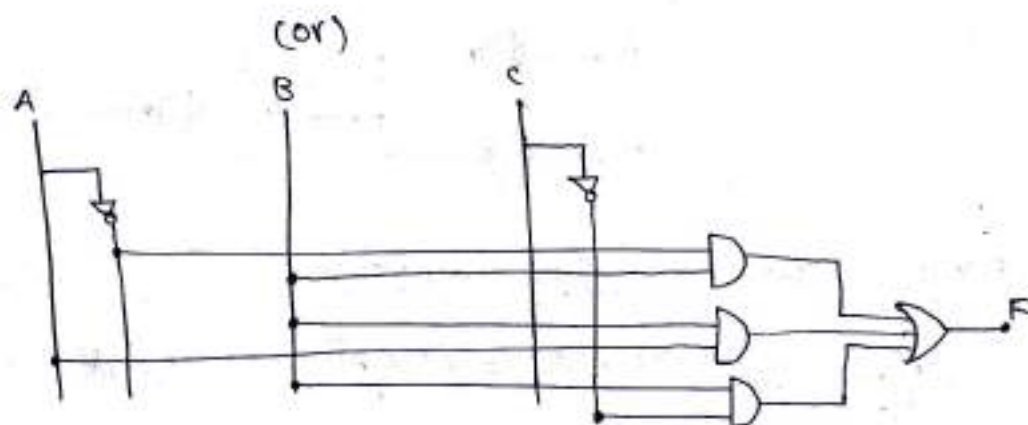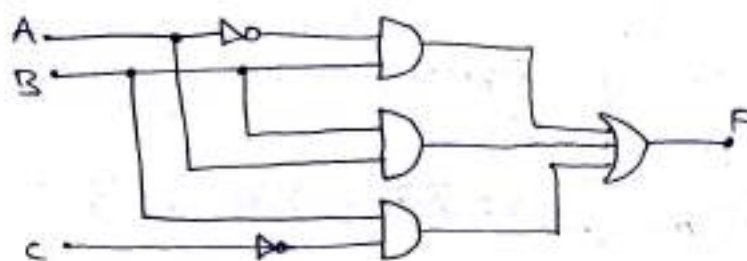

Ex:- Implement NOT, AND, OR, NOR, EXNOR, EXOR gates using NAND gate.

Sol:- NAND gate:-

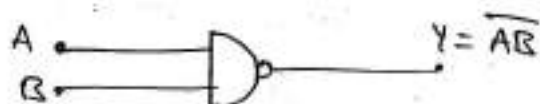



NOT gate using NAND gate:-





AND gate using NAND:-





OR gate using NAND:-

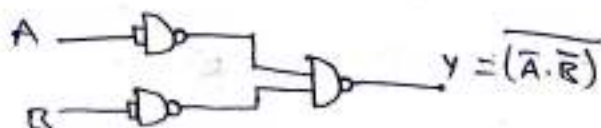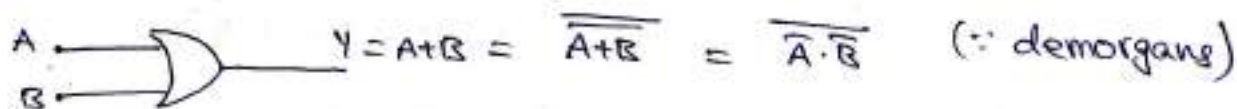

NOR gate using NAND:-

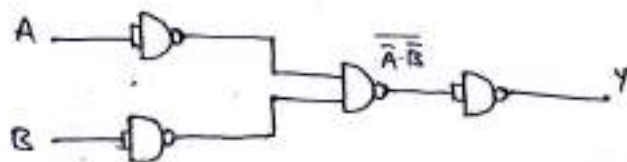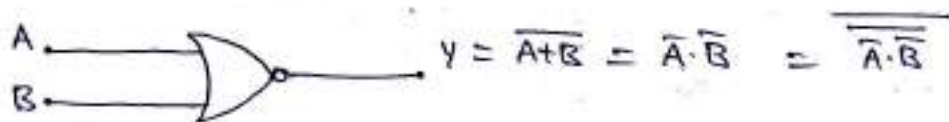


EXOR gate using NAND:-

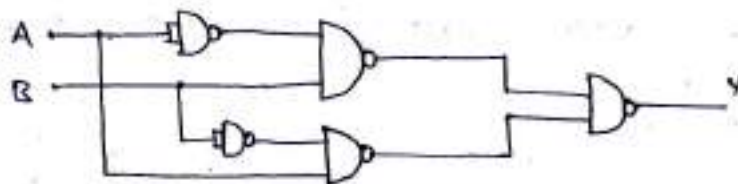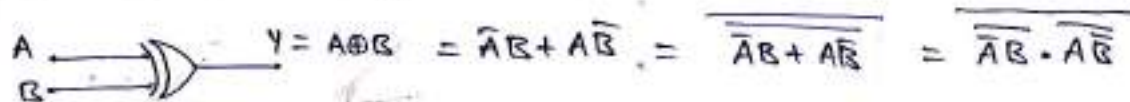



EXNOR gate using NAND:-
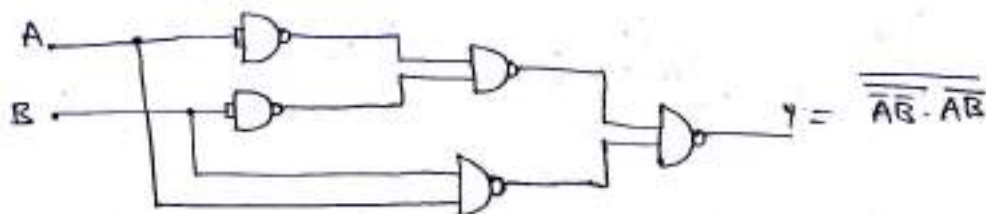
$$A \text{ --- } \text{---} B \text{ ---} \text{---} Y = A \odot B = \overline{A}B + A\overline{B} = \overline{\overline{A}B + A\overline{B}} = \overline{\overline{A}B} \cdot \overline{A\overline{B}}$$



Ex:- Implement all logic gates except NOR gate using NOR gate.



Sol:- NOR gate :-




NOT gate using NOR gate:-



AND gate using NOR gate:-

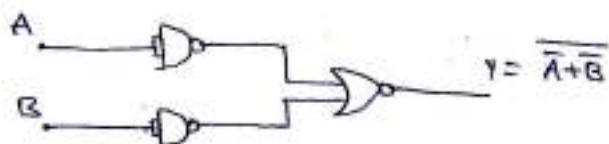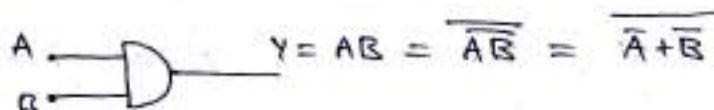


OR gate using NOR gate:-

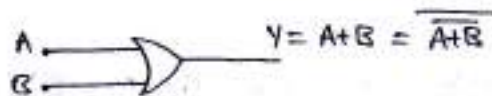

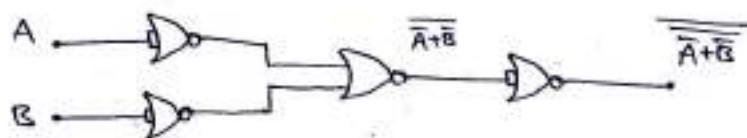
### NAND gate using NOR gate :-

$$A \text{ --- } \text{NAND} \text{ --- } B \quad \overline{AB} = \overline{A+B} = \overline{\overline{\overline{A+B}}}$$



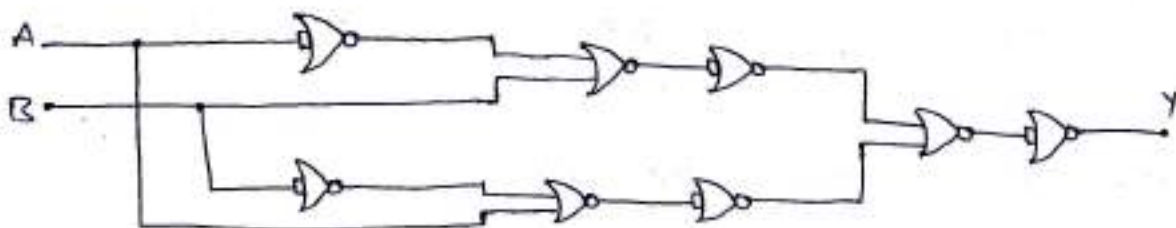
### EXOR gate using NOR gate :-

$$A \text{ --- } \text{EXOR} \text{ --- } B \quad Y = A \oplus B = \overline{A}B + A\overline{B} = \overline{\overline{\overline{A}B}} + \overline{\overline{A\overline{B}}} \\ = \overline{\overline{A}B + A\overline{B}}$$


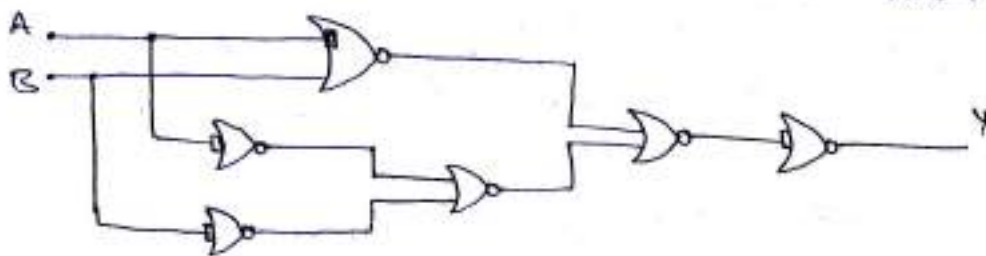
### EXNOR gate using NOR gate :-

$$A \text{ --- } \text{EXNOR} \text{ --- } B \quad Y = A \odot B = \overline{A}B + A\overline{B} = \overline{\overline{\overline{A}B}} + \overline{\overline{A\overline{B}}} = \overline{\overline{A}B + A\overline{B}} \\ = \overline{\overline{A+B} + \overline{A+B}} = \overline{\overline{A+B} \cdot \overline{A+B}} = \overline{\overline{A+B}} = A+B$$



Ex:- Implement  $F = \overline{x}y + x\overline{y} + y\overline{z}$  using (i) Basic gates


(ii) AND 4 NOT gates (iii) OR 4 NOT gates

(iv) only NAND gate (iv) only NOR gate.

Sol:


$$F = \bar{x}y + xy + y\bar{z}$$

(i) using Basic gates.

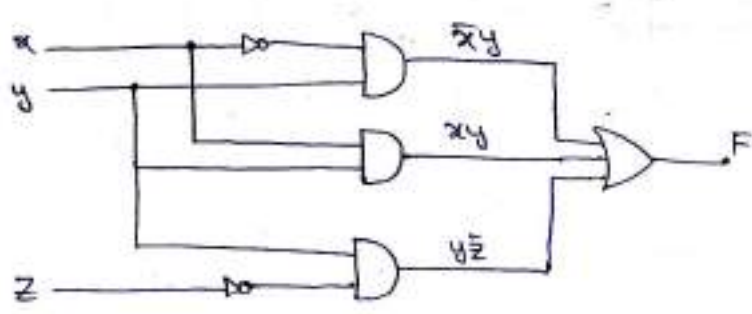

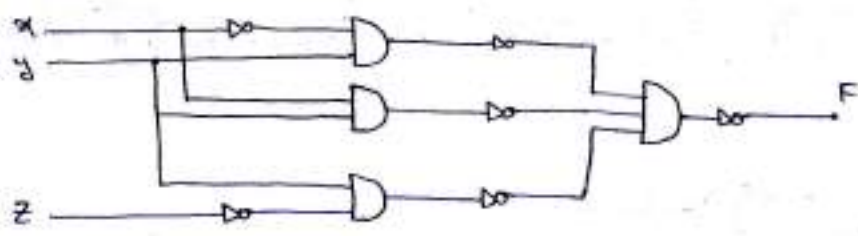
(ii) using AND & NOT gates

$$F = \bar{x}y + xy + y\bar{z} = \overline{\overline{\bar{x}y + xy + y\bar{z}}} = \overline{\bar{x}y \cdot xy \cdot y\bar{z}}$$



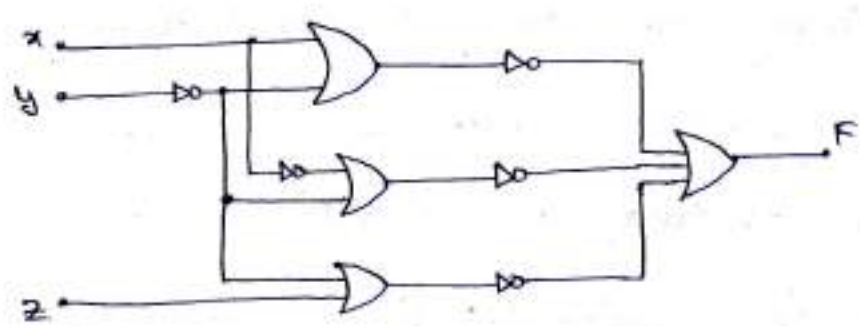(iii) using OR & NOT gates.


$$\begin{aligned} F &= \bar{x}y + xy + y\bar{z} \\ &= \overline{\bar{x}y} + \overline{xy} + \overline{y\bar{z}} \\ &= \overline{\bar{x} + \bar{y}} + \overline{x + \bar{y}} + \overline{y + \bar{z}} \\ &= \overline{x + \bar{y}} + \overline{x + \bar{y}} + \overline{y + \bar{z}} \end{aligned}$$



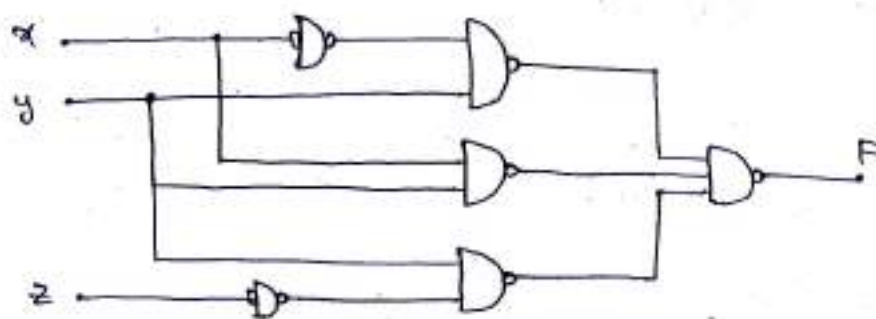(iv) using NAND gate

$$\begin{aligned} F &= \bar{x}y + xy + y\bar{z} \\ &= \overline{\overline{\bar{x}y + xy + y\bar{z}}} \quad (\because \text{demorgan's}) \\ &= \overline{\bar{x}y \cdot xy \cdot y\bar{z}} \end{aligned}$$






(v) using NOR gates.

$$F = \bar{x}y + xy + yz$$

$$= \overline{\overline{\bar{x}y}} + \overline{\overline{xy}} + \overline{\overline{yz}}$$

$$= \overline{\bar{x} + \bar{y}} + \overline{x + \bar{y}} + \overline{\bar{y} + \bar{z}}$$
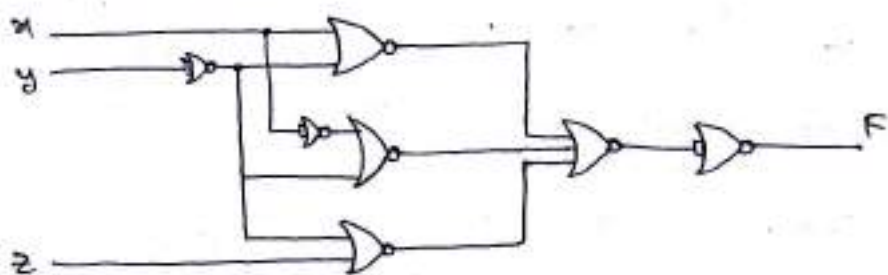
$$= \overline{x + \bar{y}} + \overline{\bar{x} + \bar{y}} + \overline{\bar{y} + \bar{z}} = \overline{\overline{x + \bar{y}} + \overline{\bar{x} + \bar{y}} + \overline{\bar{y} + \bar{z}}}$$



\* Representation of switching functions (or) logic functions

(or) Boolean function :-

There are two standard forms in which logic functions can be expressed.

(i) Sum of products form (SOP)

(ii) Product of Sum's (POS).

(i) SOP :- SOP is a group of product terms ORed together.

Ex:  $F = \bar{x}y + xy + yz$

(ii) POS:- POS is a group of sum terms ANDed together. 25

Ex:-  $F = (\bar{x} + \bar{y})(x + y)(y + z)$

Standard ~~and~~ canonical SOP & POS forms:-

In <sup>standard</sup> the ~~SOP~~ SOP & POS forms all the individual terms do not contain all variables. If each term is SOP & POS form contains all variables then it is canonical ~~standard~~ SOP & POS forms.

Ex. of CSOP is,

$$F(A, B, C) = \bar{A}BC + ABC + A\bar{B}C$$

Ex. of GPOS is,

$$F(A, B, C) = (\bar{A} + B + C)(A + B + C)(A + \bar{B} + C)$$

Ex:- convert the given expression is into <sup>canonical</sup> ~~standard~~ SOP form.

(i)  $Y(A, B, C) = \bar{A}B + A\bar{B}C$

Sol:-  
$$= \bar{A}B(C + \bar{C}) + A\bar{B}C \quad (\because C + \bar{C} = 1)$$
$$= \bar{A}BC + \bar{A}B\bar{C} + A\bar{B}C$$

(ii)  $Y(A, B, C) = AB + BC + CA$

Sol:-  
$$= AB(C + \bar{C}) + BC(A + \bar{A}) + CA(B + \bar{B})$$
$$= ABC + AB\bar{C} + ABC + \bar{A}BC + ABC + A\bar{B}C$$
$$= ABC(1 + 1 + 1) + AB\bar{C} + A\bar{B}C + \bar{A}BC \quad (\because 1 + \text{anything} = 1)$$
$$= ABC + AB\bar{C} + A\bar{B}C + \bar{A}BC$$

(iii)  $A(x, y, z) = x + xy + xyz$

Sol:-  
$$= x(y + \bar{y})(z + \bar{z}) + xy(z + \bar{z}) + xyz$$
$$= x(yz + y\bar{z} + \bar{y}z + \bar{y}\bar{z}) + xy(z + \bar{z}) + xyz$$
$$= xyz + xy\bar{z} + x\bar{y}z + x\bar{y}\bar{z} + xyz + xy\bar{z} + xyz$$
$$= xyz(1 + 1 + 1) + xy\bar{z} + x\bar{y}z + x\bar{y}\bar{z} + xy\bar{z}$$
$$= xyz + xy\bar{z} + x\bar{y}z + x\bar{y}\bar{z} + xy\bar{z}$$
$$= xyz + xy\bar{z} + x\bar{y}z + x\bar{y}\bar{z}$$



05/08/2014

Ex:- Convert the given expression into canonical POS form.

①  $F(A, B, C) = (A+B)(B+C)(A+C)$

Sol:-

$$= (A+B+C\bar{C})(B+C+A\bar{A})(A+C+B\bar{B})$$

( $\because A+B\bar{C} = (A+B)(A+\bar{C})$ )  
( $\because$  distributive)

$$= (A+B+C)(A+B+\bar{C})(B+C+A)(B+C+\bar{A})(A+C+B)(A+C+\bar{B})$$

$$= (A+B+C)(\bar{A}+B+C)(A+\bar{B}+C)(A+B+\bar{C})$$

(ii)  $F(x, y, z) = x(x+y)(x+y+\bar{z})$

Sol:-

$$= (x+y\bar{y}+z\bar{z})(x+y+z\bar{z})(x+y+\bar{z})$$

$$= (x+y\bar{y}+z)(x+y\bar{y}+\bar{z})(x+y+z)(x+y+\bar{z})(x+y+\bar{z})$$

$$= (x+y+z)(x+\bar{y}+z)(x+y+\bar{z})(x+\bar{y}+\bar{z})(x+y+z)(x+y+\bar{z})$$

$$= (x+y+z)(x+\bar{y}+z)(x+y+\bar{z})(x+\bar{y}+\bar{z})$$

### \* Minterms and Maxterms:-

→ Each individual term in CSOP is called Minterm.

→ Each individual term in CPOS is called Maxterm.

\* For 'n' variable logic function there are  $2^n$  minterms and  $2^n$  maxterms.

### Minterms and Maxterms for 3 Binary Variables:-

variables

Minterms ( $m_i$ )

Maxterm ( $M_i$ )

A B C

Term designation

Term designation

0 0 0

$\bar{A}\bar{B}\bar{C}$  —  $m_0$

$A+B+C$  —  $M_0$

0 0 1

$\bar{A}\bar{B}C$  —  $m_1$

$A+B+\bar{C}$  —  $M_1$

0 1 0

$\bar{A}B\bar{C}$  —  $m_2$

$A+\bar{B}+C$  —  $M_2$

0 1 1

$\bar{A}BC$  —  $m_3$

$A+\bar{B}+\bar{C}$  —  $M_3$

1 0 0

$A\bar{B}\bar{C}$  —  $m_4$

$\bar{A}+B+C$  —  $M_4$

1 0 1

$A\bar{B}C$  —  $m_5$

$\bar{A}+B+\bar{C}$  —  $M_5$

1 1 0

$AB\bar{C}$  —  $m_6$

$\bar{A}+\bar{B}+C$  —  $M_6$

1 1 1

$ABC$  —  $m_7$

$\bar{A}+\bar{B}+\bar{C}$  —  $M_7$



→ the minterm is represented by  $m$ , Maxterm by  $M$   
 → The subscript 'i' is the decimal number equivalent of binary input.

\* With these short hand notations, logic function can be represented as follows.

$$\begin{aligned} \text{Ex: (i)} \quad Y &= \overset{1}{A}\overset{1}{B}\overset{1}{C} + \overset{0}{A}\overset{1}{B}\overset{1}{C} + \overset{1}{A}\overset{0}{B}\overset{1}{C} + \overset{1}{A}\overset{0}{B}\overset{0}{C} \\ &= m_7 + m_3 + m_5 + m_4 \\ &= \sum m(3, 4, 5, 7) \\ &= \sum(3, 4, 5, 7) \end{aligned}$$

$\Sigma$  denotes SOP

$$\begin{aligned} \text{(ii)} \quad Y &= (\overset{0}{A} + \overset{0}{B} + \overset{0}{C})(\overset{1}{A} + \overset{0}{B} + \overset{1}{C})(\overset{1}{A} + \overset{1}{B} + \overset{1}{C}) \\ &= M_0 \cdot M_5 \cdot M_7 \\ &= \Pi M(0, 5, 7) \\ &= \Pi(0, 5, 7) \end{aligned}$$

$\Pi$  denotes POS

Note:- If o/p func is '1' then it corresponds to minterm.  
 If o/p func is '0' then it corresponds to maxterm.  
Ex:- Find SOP and POS expressions from given truth table

i/p's			o/p
A	B	C	Y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	0
1	1	1	1

Note:-

o/p is '1' → minterm

o/p is '0' → maxterm.

Sol:-

SOP

$$\begin{aligned} Y(A, B, C) &= \bar{A}\bar{B}\bar{C} + A\bar{B}C + \bar{A}B\bar{C} + ABC \\ &= m_0 + m_2 + m_3 + m_7 = \sum m(0, 2, 3, 7) \end{aligned}$$

POS

$$\begin{aligned} Y(A, B, C) &= (A+B+\bar{C})(\bar{A}+B+C)(\bar{A}+B+\bar{C})(\bar{A}+\bar{B}+C) \\ &= M_1 \cdot M_4 \cdot M_5 \cdot M_6 = \Pi M(1, 4, 5, 6) \end{aligned}$$

\* From the above expressions, there is a complementary

Ex: Simplify the following 3 variable expressions using boolean algebra.

(i)  $Y = \sum m(1, 3, 5, 7)$  considering  $A, B, C$  as 3 IP variables.

Sol:

$$\begin{aligned} Y &= m_1 + m_3 + m_5 + m_7 \\ &= \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + ABC \\ &= \bar{A}C(B + \bar{B}) + AC(B + \bar{B}) \\ &= \bar{A}C + AC \quad (\because A + \bar{A} = 1) \\ &= C(A + \bar{A}) = C \end{aligned}$$

(ii)  $Y = \prod M(3, 7)$

Sol:

$$\begin{aligned} Y &= M_3 \cdot M_7 \\ &= (A + \bar{B} + \bar{C})(\bar{A} + \bar{B} + \bar{C}) \\ &= A \cdot \bar{A} + A \cdot \bar{B} + A \cdot \bar{C} + \bar{A} \cdot \bar{B} + \bar{B} + \bar{B} \cdot \bar{C} + \bar{C} \cdot \bar{A} + \bar{B} \bar{C} + \bar{C} \\ &= A\bar{B} + A\bar{C} + \bar{A}\bar{B} + \bar{B} + \bar{B}\bar{C} + \bar{C}\bar{A} + \bar{C} \\ &= \bar{B}(A + \bar{A}) + \bar{C}(A + \bar{A}) + \bar{B}(1 + \bar{C}) + \bar{C} \\ &= \bar{B} + \bar{C} + \bar{B} + \bar{C} \quad (\because 1 + \text{anything} = 1) \\ &= \bar{B} + \bar{C} \end{aligned}$$

Ex: Convert the given expression into minterms using complementary property, and simplify the expression.

(i)  $F = \prod M(3, 5, 7)$

Sol:  $F = M_3 \cdot M_5 \cdot M_7 \rightarrow$  This is POS form.

$\therefore$  SOP form is,

$$\begin{aligned} F(A, B, C) &= \sum m(0, 1, 2, 4, 6) \\ &= m_0 + m_1 + m_2 + m_4 + m_6 \\ &= \bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}\bar{C} + AB\bar{C} \\ &= \bar{A}\bar{B}(C + \bar{C}) + \bar{A}B\bar{C} + A\bar{C}(B + \bar{B}) \\ &= \bar{A}\bar{B} + \bar{A}B\bar{C} + A\bar{C} \end{aligned}$$



$$\begin{aligned}
 &= \bar{A}\bar{B} + \bar{C}(\bar{A}B + A) && (\because \text{distributive law}) \\
 &= (\bar{A}\bar{B} + \bar{C})(\bar{A}\bar{B} + \bar{A}B + A) \\
 &= (\bar{A}\bar{B} + \bar{C})(\bar{A}(B + \bar{B}) + A) \\
 &= (\bar{A}\bar{B} + \bar{C})(A + \bar{A}) = \bar{A}\bar{B} + \bar{C}
 \end{aligned}$$

Ex:- Express the following functions in sum of minterms (canonical SOP) and product of max. terms (canonical POS) forms.

(i)  $F(w, x, y, z) = w'y + xy' + yz + xyz$

Sol:-

<u>w'y</u>			
w'	y		
0	0	1	0 — m <sub>2</sub>
0	0	1	1 — m <sub>3</sub>
0	1	1	0 — m <sub>6</sub>
0	1	1	1 — m <sub>7</sub>

<u>xy</u>			
w	x	y'	z
0	1	0	0 — m <sub>4</sub>
0	1	0	1 — m <sub>5</sub>
1	1	0	0 — m <sub>12</sub>
1	1	0	1 — m <sub>13</sub>

<u>yz</u>			
w	x	y	z
0	0	1	1 — m <sub>3</sub>
0	1	1	1 — m <sub>7</sub>
1	0	1	1 — m <sub>11</sub>
1	1	1	1 — m <sub>15</sub>

<u>xyz</u>			
w	x	y	z
0	1	1	1 — m <sub>7</sub>
1	1	1	1 — m <sub>15</sub>

CSOP (or) Sum of minterms form,

$$\begin{aligned}
 F(w, x, y, z) &= m_2 + m_3 + m_4 + m_5 + m_6 + m_7 + m_{11} + m_{12} + m_{13} + m_{15} \\
 &= \sum m(2, 3, 4, 5, 6, 7, 11, 12, 13, 15)
 \end{aligned}$$

Remaining terms are maxterms.

CPOS (or) Product of maxterms form.

$$\begin{aligned}
 F(w, x, y, z) &= M_0 \cdot M_1 \cdot M_8 \cdot M_9 \cdot M_{10} \cdot M_{14} \\
 &= \prod M(0, 1, 8, 9, 10, 14)
 \end{aligned}$$



②  $F(A, B, C) = (AB + C)(AC + B)$

Sol:-  $F(A, B, C) = ABC + AB + AC + BC$

$\begin{array}{c|ccc} & \overline{A} & A & \\ \hline \overline{B} & & & \\ B & & & \end{array}$   
 $A \ B \ C$   
 $1 \ 1 \ 1 \rightarrow m_7$

$\begin{array}{c|ccc} & \overline{A} & A & \\ \hline \overline{B} & & & \\ B & & & \end{array}$   
 $A \ B \ C$   
 $1 \ 1 \ 0 \rightarrow m_6$   
 $1 \ 1 \ 1 \rightarrow m_7$

$\begin{array}{c|ccc} & \overline{A} & A & \\ \hline \overline{B} & & & \\ B & & & \end{array}$   
 $A \ B \ C$   
 $0 \ 1 \ 1 \rightarrow m_3$   
 $1 \ 1 \ 1 \rightarrow m_7$

$\begin{array}{c|ccc} & \overline{A} & A & \\ \hline \overline{B} & & & \\ B & & & \end{array}$   
 $A \ B \ C$   
 $1 \ 0 \ 1 \rightarrow m_5$   
 $1 \ 1 \ 1 \rightarrow m_7$

Sum of minterms  $F = \sum m(3, 5, 6, 7)$

Product of maxterms  $F = \prod M(0, 1, 2, 4)$

06/08/2014

\* Karnaugh Map (K-Map) :-

K-Map gives a systematic approach for simplifying a boolean expression. The basis of this method is a graphical chart known as "K-Map". It contains boxes called cells. Each of the cell represents one of the  $2^n$  possible products that can be formed from 'n' variables.

2-variable K-Map

(i) Representation using

$\overline{A}$	$\overline{B}$	$B$
$\overline{A}$	$\overline{A}\overline{B}$	$\overline{A}B$
$A$	$A\overline{B}$	$AB$

2-variable K-Map representation using minterms

$\overline{A}$	$\overline{B}$	$B$
$\overline{A}$	$m_0$ 00	$m_1$ 01
$A$	$m_2$ 10	$m_3$ 11

2-variable K-Map representation using maxterms

(ii) Representation using maxterms

$\overline{A}$	$\overline{B}$	$B$
$\overline{A}$	$M_0$ 00	$M_1$ 01
$A$	$M_2$ 10	$M_3$ 11

$\overline{A}$	$\overline{B}$	$B$
$\overline{A}$	$M_0$ 00	$M_1$ 01
$A$	$M_2$ 10	$M_3$ 11

Ex:- (i) Simplify  $F(A,B) = \sum m(0,1)$  using K-Map.

Sol:-

A \ B	0	1
0	1	1
1	0	0

$$F(A,B) = \sum m(0,1)$$

$$= m_0 + m_1$$

Fill minterms with '1'.

$$\therefore F(A,B) = \bar{A}$$

$$(\because F(A,B) = \bar{A}\bar{B} + \bar{A}B$$

$$= \bar{A}(B + \bar{B}) = \bar{A})$$

(ii) Simplify  $F(A,B) = \sum m(0,2)$  using K-Map.

Sol:-

A \ B	0	1
0	1	0
1	1	0

$$F(A,B) = \sum m(0,2)$$

$$= m_0 + m_2$$

$$\therefore F(A,B) = \bar{B}$$

(iii) Simplify  $F(A,B) = \sum (0,3)$  using K-Map.

Sol:-

A \ B	0	1
0	1	0
1	0	1

$$F(A,B) = \sum (0,3)$$

$$= \sum m(0,3)$$

$$= m_0 + m_3$$

$$\therefore F(A,B) = \bar{A}\bar{B} + AB$$

(iv) Simplify  $F(A,B) = \prod M(1,3)$  using K-Map.

Sol:-

A \ B	0	1
0	0	1
1	0	1

$$F(A,B) = \prod M(1,3)$$

$$= M_1 + M_3$$

Fill maxterms with '0's.

$$\therefore F(A,B) = \bar{B}$$

(v) Simplify  $F(x,y) = \prod (1,2)$  using K-Map.

Sol:-

x \ y	0	1
0	0	1
1	1	0

$$F(x,y) = \prod (1,2)$$

$$= M_1 + M_2$$

Fill maxterms with '0's.

$$\therefore F(x,y) = (x + \bar{y})(\bar{x} + y)$$



### 3- Variable K-Map :-

Representation using minterms

A \ BC	$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	$BC$
$\bar{A}$	$\bar{A}\bar{B}\bar{C}$	$\bar{A}\bar{B}C$	$\bar{A}B\bar{C}$	$\bar{A}BC$
A	$A\bar{B}\bar{C}$	$A\bar{B}C$	$AB\bar{C}$	$ABC$

A \ BC	00	01	11	10
0	$m_0$	$m_1$	$m_3$	$m_2$
1	$m_4$	$m_5$	$m_7$	$m_6$

Representation using maxterms

A \ BC	$B+C$	$B+\bar{C}$	$\bar{B}+C$	$\bar{B}+\bar{C}$
A	$A+B+C$	$A+B+\bar{C}$	$A+\bar{B}+C$	$A+\bar{B}+\bar{C}$
$\bar{A}$	$\bar{A}+B+C$	$\bar{A}+B+\bar{C}$	$\bar{A}+\bar{B}+C$	$\bar{A}+\bar{B}+\bar{C}$

A \ BC	00	01	11	10
0	$M_0$	$M_1$	$M_3$	$M_2$
1	$M_4$	$M_5$	$M_7$	$M_6$

Ex: ① Simplify  $F(A,B,C) = \sum m(1,5,2,6)$  using K-Map.

Sol:

A \ BC	$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	$BC$
$\bar{A}$	0	1	3	2
A	4	5	7	6

$$F(A,B,C) = \sum m(1,5,2,6)$$

$$= m_1 + m_2 + m_5 + m_6$$

Fill minterms with '1's.

$$\therefore F(A,B,C) = \bar{B}C + B\bar{C}$$

$$\therefore F(A,B,C) = B \oplus C$$

$$(\because F(A,B,C) = \bar{A}\bar{B}C + \bar{A}B\bar{C} + A\bar{B}C + AB\bar{C})$$

$$= \bar{B}C(A+\bar{A}) + B\bar{C}(A+\bar{A})$$

$$= \bar{B}C + B\bar{C}$$

$$= B \oplus C$$

(ii) Simplify  $F(A,B,C) = \sum (1,3,5,7,6)$  using K-map.

Sol:

A \ BC	$\bar{B}\bar{C}$	$\bar{B}C$	$B\bar{C}$	$BC$
$\bar{A}$	0	1	3	2
A	4	5	7	6

$$F(A,B,C) = \sum (1,3,5,7,6)$$

$$= m_1 + m_3 + m_5 + m_6 + m_7$$

Fill minterms with '1's.

$$\therefore F(A,B,C) = C + BA$$



(iii)  $F(A, B, C) = \sum (0, 1, 4, 5, 2, 6)$ .

Sol:-

A \ BC	$\bar{B}\bar{C}$ 00	$\bar{B}C$ 01	$B\bar{C}$ 11	$BC$ 10
$\bar{A}$ 0	1	1		1
A 1	1	1		1

$\therefore F(A, B, C) = \bar{B} + \bar{C}$ .

$F(A, B, C) = m_0 + m_1 + m_2 + m_4 + m_5 + m_6$ .

(iv)  $F(x, y, z) = \sum m(0, 1, 2, 3, 5)$ .

Sol:-

x \ yz	$\bar{y}\bar{z}$ 00	$\bar{y}z$ 01	$y\bar{z}$ 11	$yz$ 10
0	1	1	1	1
1		1		

$\therefore F(x, y, z) = \bar{x} + \bar{y}z$

(v)  $F(x, y, z) = \sum (1, 4, 5, 6)$ .

Sol:-

x \ yz	$\bar{y}\bar{z}$ 00	$\bar{y}z$ 01	$y\bar{z}$ 11	$yz$ 10
0 $\bar{x}$		1		
1 x	1	1		1

$\therefore F(x, y, z) = \bar{y}z + x\bar{z}$

don't care condition

$x \rightarrow$  don't care symbol, it can be 0 or 1.

(vi)  $y(A, B, C) = \sum m(1, 3, 5) + \sum d(6, 7)$ .

Sol:-

A \ BC	$\bar{B}\bar{C}$ 00	$\bar{B}C$ 01	$B\bar{C}$ 11	$BC$ 10
$\bar{A}$ 0		1	1	
A 1		1	X	X

$y(A, B, C) = m_1 + m_3 + m_5 + d_6 + d_7$

Fill minterms with '1'.

Fill don't terms with 'x'.

It may be '0' or '1'.

consider  $d_7 = 1$ .

$\therefore y(A, B, C) = C$

Ex:- Simplify the following boolean expression and draw logic circuit.

(vii)  $Y(A, B, C) = \sum(0, 1, 2, 6)$

Sol:-


A \ BC	$\bar{B}\bar{C}$		$\bar{B}C$		$BC$		$B\bar{C}$	
	00	01	11	10	00	01	11	10
$\bar{A}$ 0	1	1					1	
A 1							1	

$$Y(A, B, C) = \sum(0, 1, 2, 6)$$

$$= m_0 + m_1 + m_2 + m_6$$

$$\therefore Y(A, B, C) = \bar{A}\bar{B} + B\bar{C}$$

logic circuit:-

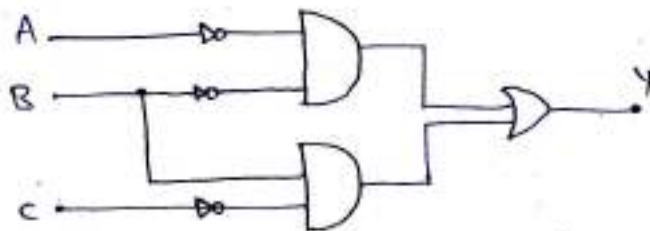

Ex:- Simplify the following boolean expression and draw logic circuits using NAND gate only.

(viii)  $F = \sum(0, 1, 5, 6) + \sum d(4, 3)$

Sol:-

A \ BC	$\bar{A}\bar{B}$		$\bar{A}B$		$A\bar{B}$		$AB$	
	00	01	11	10	00	01	11	10
$\bar{A}$ 0	1	1	X					
A 1	X	1					1	


$$F = m_0 + m_1 + m_5 + m_6 + d_3 + d_4$$

Fill minterms with 1's  
Fill don't terms with x's

$$F = \bar{B} + A\bar{C} = A\bar{C} + \bar{B}$$

logic circuit:-
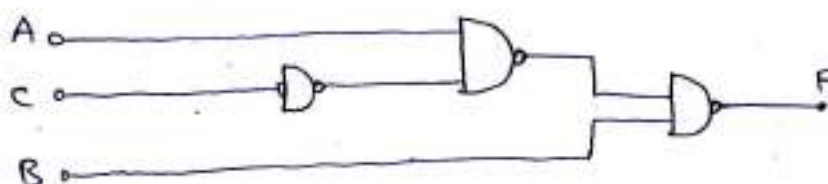
$$F = A\bar{C} + \bar{B} = \overline{\overline{A\bar{C}} + \overline{\bar{B}}} = \overline{\bar{B} \cdot A\bar{C}} = \overline{B \cdot A\bar{C}}$$





07/08/2014

30

(ix)

$$F(A, B, C) = \pi M(0, 1, 3, 4, 7)$$

Sol.

A \ BC	00		01		11		10	
	$\bar{B} + \bar{C}$		$\bar{B} + \bar{C}$		$\bar{B} + \bar{C}$		$\bar{B} + \bar{C}$	
0 A	0	0	0	0	0	0	0	0
1 $\bar{A}$	0	0	0	0	0	0	0	0

$$F(A, B, C) = \pi M(0, 1, 3, 4, 7)$$

$$= M_0 \cdot M_1 \cdot M_3 \cdot M_4 \cdot M_7$$

Fill maxterms with 0's.

$$\therefore F(A, B, C) = (B + C)(\bar{B} + \bar{C})(A + \bar{C})$$

(or)

$$(B + C)(\bar{B} + \bar{C})(A + B)$$

$$(x) F = \pi M(0, 1, 3, 7) + \pi d(2, 5)$$

Sol.

A \ BC	00		01		11		10	
	$\bar{B} + \bar{C}$		$\bar{B} + \bar{C}$		$\bar{B} + \bar{C}$		$\bar{B} + \bar{C}$	
0 A	0	0	0	0	0	0	0	0
1 $\bar{A}$	0	0	0	0	0	0	0	0

$$F = \pi M(0, 1, 3, 7) + \pi d(2, 5)$$

$$= M_0 \cdot M_1 \cdot M_3 \cdot M_7 + d_2 d_5$$

Fill maxterms with 0's.

Fill don't terms with 'x's

consider  $d_2, d_5$  as 0's.

$$\therefore F(A, B, C) = A\bar{C}$$

$$(xi) \text{ Given } F = \sum (0, 3, 4, 7). \text{ Find (a) } F \text{ (b) dual of } F \text{ (c) } F'$$

Sol.

A \ BC	00		01		11		10	
	$\bar{B} + \bar{C}$		$\bar{B} + \bar{C}$		$\bar{B} + \bar{C}$		$\bar{B} + \bar{C}$	
0 $\bar{A}$	0	0	0	0	0	0	0	0
1 A	0	0	0	0	0	0	0	0

$$F = \sum m(0, 3, 4, 7)$$

$$= m_0 + m_3 + m_4 + m_7$$

Fill minterms with 1's.

$$F \rightarrow \text{POS SOP}$$

$$(i) F(A, B, C) = \bar{B}\bar{C} + B\bar{C} = B\bar{C}$$

$$(ii) \text{ Dual of } F \text{ is } (\bar{B} + \bar{C})(B + C)$$

$$= B \cdot \bar{B} + C \cdot \bar{B} + \bar{C} \cdot B + C \cdot \bar{C}$$

$$= B\bar{C} + \bar{B}C = B\bar{C}$$

$$\therefore \boxed{\text{Dual of } F = B\bar{C} + \bar{B}C = B\bar{C}}$$

$$(iii) F' \rightarrow \text{SOP}$$

$$\therefore F' = \pi(1, 2, 5, 6)$$

$$\therefore F' = (\bar{B} + C)(B + C')$$

$$(\because F' = \text{dual of } F)$$



## 4-variable K-Map :-

Representation using Minterms

AB \ CD	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$	$\bar{A}\bar{B}\bar{C}\bar{D}$	$\bar{A}\bar{B}\bar{C}D$	$\bar{A}\bar{B}C\bar{D}$	$\bar{A}\bar{B}CD$
$\bar{A}B$	$\bar{A}B\bar{C}\bar{D}$	$\bar{A}B\bar{C}D$	$\bar{A}B C\bar{D}$	$\bar{A}B CD$
$A\bar{B}$	$A\bar{B}\bar{C}\bar{D}$	$A\bar{B}\bar{C}D$	$A\bar{B} C\bar{D}$	$A\bar{B} CD$
$AB$	$AB\bar{C}\bar{D}$	$AB\bar{C}D$	$AB C\bar{D}$	$AB CD$

AB \ CD	00	01	11	10
00	$m_0$	$m_1$	$m_3$	$m_2$
01	$m_4$	$m_5$	$m_7$	$m_6$
11	$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$
10	$m_8$	$m_9$	$m_{11}$	$m_{10}$

Representation using maxterms

AB \ CD	$C+D$	$C+\bar{D}$	$\bar{C}+D$	$\bar{C}+\bar{D}$
$\bar{A}+\bar{B}$	$\bar{A}+\bar{B}+C+D$	$\bar{A}+\bar{B}+C+\bar{D}$	$\bar{A}+\bar{B}+\bar{C}+D$	$\bar{A}+\bar{B}+\bar{C}+\bar{D}$
$\bar{A}+B$	$\bar{A}+B+C+D$	$\bar{A}+B+C+\bar{D}$	$\bar{A}+B+\bar{C}+D$	$\bar{A}+B+\bar{C}+\bar{D}$
$A+\bar{B}$	$A+\bar{B}+C+D$	$A+\bar{B}+C+\bar{D}$	$A+\bar{B}+\bar{C}+D$	$A+\bar{B}+\bar{C}+\bar{D}$
$A+B$	$A+B+C+D$	$A+B+C+\bar{D}$	$A+B+\bar{C}+D$	$A+B+\bar{C}+\bar{D}$

AB \ CD	00	01	11	10
00	$M_0$	$M_1$	$M_3$	$M_2$
01	$M_4$	$M_5$	$M_7$	$M_6$
11	$M_{12}$	$M_{13}$	$M_{15}$	$M_{14}$
10	$M_8$	$M_9$	$M_{11}$	$M_{10}$

Ex: (i)  $F(A, B, C, D) = \sum m(2, 4, 5, 9, 10, 12, 13)$

Sol:

AB \ CD	$\bar{C}\bar{D}$	$\bar{C}D$	$CD$	$C\bar{D}$
$\bar{A}\bar{B}$ 00				1
$\bar{A}B$ 01	1	1		
$AB$ 11	1	1		
$A\bar{B}$ 10		1		1

$$F(A, B, C, D) = \sum m(2, 4, 5, 9, 10, 12, 13)$$

$$= m_2 + m_4 + m_5 + m_9 + m_{10} + m_{12} + m_{13}$$

Fill Minterms with 1's.

$$\therefore F(A, B, C, D) = \bar{B}\bar{C} + A\bar{C}D + \bar{B}C\bar{D}$$

(ii)  $F(w, x, y, z) = \sum m(1, 3, 5, 7, 8, 9, 10, 11, 12, 14)$

Sol:

$w \backslash x$	$y \bar{z}$	$\bar{y} \bar{z}$	$\bar{y} z$	$y z$
$\bar{w} \bar{x}$ 00	0	1	1	2
$\bar{w} x$ 01	4	1	1	6
$w \bar{x}$ 11	1	12	13	14
$w x$ 10	1	8	9	10

$$F(w, x, y, z) = m_1 + m_3 + m_5 + m_7 + m_8 + m_9 + m_{10} + m_{11} + m_{12} + m_{14}$$

fill minterms with 1's.

$$F(w, x, y, z) = z\bar{w} + w\bar{z} + w\bar{x} \\ = w\bar{x} + w\bar{z} + \bar{w}z$$

(iii)  $F(A, B, C, D) = \sum (0, 1, 2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$

Sol:

$AB \backslash CD$	$\bar{C}\bar{D}$ 00	$\bar{C}D$ 01	$CD$ 11	$C\bar{D}$ 10
$\bar{A}\bar{B}$ 00	1	1	1	1
$\bar{A}B$ 01	4	1	1	6
$AB$ 11	12	1	1	14
$A\bar{B}$ 10	1	1	1	1

$$F(A, B, C, D) = m_0 + m_1 + m_2 + m_3 + m_5 + m_7 + m_8 + m_9 + m_{10} + m_{11} + m_{13} + m_{15}$$

fill minterms with 1's.

$$F(A, B, C, D) = D + \bar{B}$$

(iv)  $F = \sum (0, 5, 7, 8, 10, 15) + \sum d(2, 6, 13)$

Sol:

$AB \backslash CD$	$\bar{C}\bar{D}$ 00	$\bar{C}D$ 01	$CD$ 11	$C\bar{D}$ 10
$\bar{A}\bar{B}$ 00	1	1	1	X
$\bar{A}B$ 01	4	1	1	X
$AB$ 11	12	X	1	14
$A\bar{B}$ 10	1	9	11	10

$$F = \sum (0, 5, 7, 8, 10, 15) + \sum d(2, 6, 13) \\ = m_0 + m_5 + m_7 + m_8 + m_{10} + m_{15} + d_2 + d_6 + d_{13}$$

fill minterms with 1's.  
fill don't terms with x's.  
consider  $d_{13}, d_2$  as 1's.

$$\therefore F(A, B, C, D) = BD + \bar{B}\bar{D} = B \odot D$$

(v)  $F = \sum (0, 1, 2, 4, 5, 6, 7, 13, 15) + \sum \phi(3, 12, 14, 9, 11)$

Sol:

$$F = m_0 + m_1 + m_2 + m_4 + m_5 + m_6 + m_7 + m_{13} + m_{15} + \phi_3 + \phi_{12} + \phi_{14} + \phi_9 + \phi_{11}$$

fill minterms with 1's.

consider  $\phi_3, \phi_{11}$  as 1's.



AB \ CD	00	01	11	10
$\bar{A}\bar{B}$ 00	1	1	X	1
$\bar{A}B$ 01	1	1	1	1
$AB$ 11	X	1	1	X
$A\bar{B}$ 10		X	X	

$$\therefore F(A, B, C, D) = \bar{A} + D.$$

(or)

$$\bar{A} + B.$$

(vi)  $F = \sum m(1, 5, 8, 15, 13, 14) + \sum d(6, 7)$

Sol:

AB \ CD	00	01	11	10
$\bar{A}\bar{B}$ 00		1		
$\bar{A}B$ 01		1	X	X
$AB$ 11		1	1	1
$A\bar{B}$ 10	1			

$$F = m_1 + m_5 + m_8 + m_{15} + m_{13} + m_{14} + d_6 + d_7$$

Fill 'd' terms with x's  
consider  $d_6, d_7$  as 1's.

$$\therefore F(A, B, C, D) = BD + BC + \bar{A}\bar{C}D + A\bar{B}\bar{C}\bar{D}$$

(vii)  $F = \prod M(0, 4, 7, 10) + \prod d(3, 13)$

Sol:

AB \ CD	00	01	11	10
$A+B$ 00	0		X	
$A+\bar{B}$ 01	0		0	
$\bar{A}+B$ 11		X		
$\bar{A}+\bar{B}$ 10				0

$$F = M_0 \cdot M_4 \cdot M_7 \cdot M_{10} + d_3 \cdot d_{13}$$

consider  $d_3$  as 0.

$$\therefore F(A, B, C, D) = (A + C + D)(A + \bar{C} + \bar{D})(\bar{A} + B + \bar{C} + D)$$



(viii)  $F(w, x, y, z) = \pi(0, 3, 4, 7, 8, 11, 12, 14) + \pi d(2, 6)$

Sol:-

wx \ yz	00	01	11	10
w+x 00	0	1	3	X
w+x 01	0	4	5	X
w+x 11	0	2	9	10
w+x 10	0	8	11	14

$F(w, x, y, z) = M_0 \cdot M_3 \cdot M_4 \cdot M_7 \cdot M_8 \cdot M_{11} \cdot M_{12} \cdot M_{14} + d_2 \cdot d_6$

Fill maxterms with 0's.  
Fill d terms with x's.  
consider  $d_2, d_6$  as 0's.

$\therefore F(w, x, y, z) = (y+z)(\bar{x} + z)(x+y+\bar{z})$

12/08/2014

### 5-variable K-Map :-

Representing using minterms & maxterms

AB \ CDE	000	001	011	010	110	111	101	100
00	0	1	3	2	6	7	5	4
01	8	9	11	10	14	15	13	12
11	24	25	27	26	30	31	29	28
10	16	17	19	18	22	23	21	20

Ex:- Simplify the following boolean expressions using K-map.

(i)  $F = \pi M(0, 1, 4, 5, 9, 11, 13, 15, 16, 17, 25, 27, 28, 29, 31) + \pi d(20, 21, 22, 30)$

Sol:-

AB \ CDE	000	001	011	010	110	111	101	100
00	0	1	3	2	6	7	5	4
01	8	9	11	10	14	15	13	12
11	24	25	27	26	X	31	29	28
10	16	17	19	18	X	30	21	20

$\therefore F = (\bar{B} + \bar{E})(B + D)(\bar{A} + \bar{C} + D)$

(ii)  $F = \sum m(0, 2, 4, 6, 9, 11, 13, 15, 17, 21, 25, 27, 29, 31)$

Sol:-

AB \ CDE	CDE	$\bar{C}DE$	$C\bar{D}E$	$\bar{C}\bar{D}E$	$CDE$	$\bar{C}DE$	$C\bar{D}E$	$\bar{C}\bar{D}E$
AB	000	001	011	010	110	111	101	100
$\bar{A}\bar{B}$ 00	0	1	3	2	6	7	5	4
$\bar{A}B$ 01		8	9	11	10	14	15	13
$AB$ 11	24	25	27	26	30	31	29	28
$A\bar{B}$ 10	16	17	19	18	22	23	21	20

$$\therefore F = BE + A\bar{D}E + \bar{A}\bar{B}\bar{D}\bar{E}$$

Note:- (i) In K-map pair is a group of two adjacent cells which cancels one variable.

(ii) Quad is a group of 4 adjacent cells which cancels two variables.

(iii) Octet is a group of 8 adjacent cells which cancels three variables.

Ex:- ① Using demorgan's law simplify the following.

(i)  $Y_1 = ((a+b')(c'+d))'$

Sol:-  $Y_1 = \overline{(a+b')(c'+d)}$

$$= (\overline{a+b}) + (\overline{c'+d})$$

$$= (\bar{a} \cdot \bar{b}) + (\bar{c} \cdot \bar{d})$$

$$= (\bar{a} \cdot \bar{b}) + (c \cdot d)$$

$$\therefore \boxed{Y_1 = \bar{a} \cdot \bar{b} + c \cdot d}$$

( $\because$  demorgan's law

$$\overline{x+y} = \bar{x} \cdot \bar{y}$$

$$\overline{xy} = \bar{x} + \bar{y})$$

(ii)  $Y_2 = (a+b)'$

Sol:-  $Y_2 = (a+b)'$

$$= \bar{a} \cdot \bar{b} = \bar{a} \cdot b$$

$$\boxed{Y_2 = \bar{a} \cdot b}$$



Ex: ② simplify the following expressions and implement

35

using 2-level NAND gate

(i)  $AB' + ABD + ABD' + A'c'D' + A'BC'$

$(\because A+BC = (A+B)(A+C))$

Sol.  $AB' + AB(D+D') + A'c'D' + A'BC'$

$= AB' + AB + A'c'D' + A'BC'$

$= A + A'c'D' + A'BC' = (A+A')(A+c'D') + A'BC'$


$= (A + A'c'D' + A'BC')$   $= A + c'D' + A'BC'$

$= (A+A')(A+BC') + c'D'$


$= A + BC' + c'D'$

$= ((A + BC' + c'D'))'$

$= \overline{A \cdot BC' \cdot c'D'}$

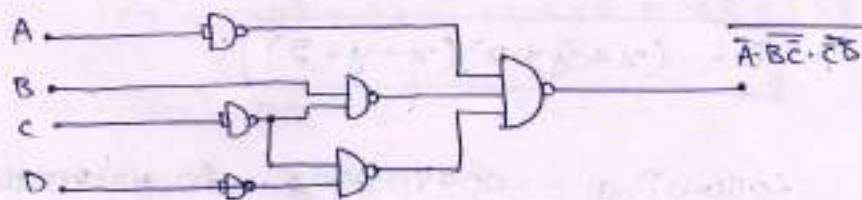

(or)

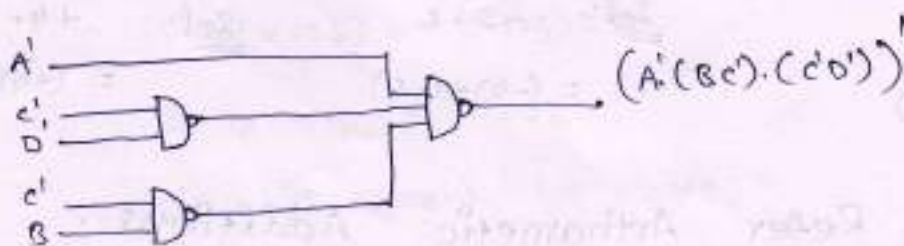

Note:-


if variables — n

$\therefore$  Total number of Maxterm  $= 2^n$

" " " Minterms  $= 2^n$

" " " Boolean expressions  $= 2^{2^n}$

Ex: ③ The minimum number of NAND gates required to implement  $A + AB' + ABC'$ .

Sol:  $A(1 + \bar{B} + B\bar{C})$  ( $\because 1 + \text{anything} = 1$ )  
 $= A$  

$\therefore$  the no. of NAND gates required = 0

④ Find complement of  $F = \bar{x}y\bar{z} + \bar{x}\bar{y}z$

Sol:  $F = \bar{x}y\bar{z} + \bar{x}\bar{y}z$

complement of F is  $\bar{F} = \overline{\bar{x}y\bar{z} + \bar{x}\bar{y}z}$   
 $= \overline{\bar{x}y\bar{z}} \cdot \overline{\bar{x}\bar{y}z}$   
 $= (\bar{x} + y + z)(\bar{x} + \bar{y} + \bar{z})$   
 $= (x + \bar{y} + z)(x + y + \bar{z})$

$\therefore \boxed{\bar{F} = (x + \bar{y} + z)(x + y + \bar{z})}$

⑤ Perform the following operations in 2's complement form.  
8-bit Binary arithmetic.

(i)  $+6 - 3$

(ii)  $-2 - 6$

(iii)  $+4 - 7$

Sol:  $+6 - 3$   
 $= (+6) + (-3)$

Sol:  $-2 - 6$   
 $= (-2) + (-6)$

Sol:  $+4 - 7$   
 $= (+4) + (-7)$

Refer Arithmetic Additions.

Page no : - ⑪



⑥ Determine the value of Base  $x$ .

(i)  $(211)_x = (152)_8$  convert both numbers into decimal.

Sol:-  $2x^2 + 1x^1 + 1x^0 = 1 \times 8^2 + 5 \times 8 + 2 \times 8^0$

$$\Rightarrow 2x^2 + x + 1 = 64 + 40 + 2$$

$$\therefore 2x^2 + x - 105 = 0$$

$$2x^2 + 15x - 14x - 105 = 0$$

$$2x(x-7) + 15(x-7) = 0$$

$$(x-7)(2x+15) = 0$$

$$\therefore x = 7 \text{ (or) } -\frac{15}{2}$$

It can't be 've'

$$\therefore \boxed{x = 7}$$

(ii)  $(193)_x = (623)_8$

Sol:-  $1x^2 + 9x^1 + 3x^0 = 6 \times 8^2 + 2 \times 8^1 + 3 \times 8^0$

$$\Rightarrow x^2 + 9x + 3 = 384 + 16 + 3$$

$$\therefore x^2 + 9x - 400 = 0$$

$$x^2 + 25x - 16x - 400 = 0$$

$$x(x+25) - 16(x+25) = 0$$

$$\therefore x = 16 \text{ (or) } -25$$

It can't be 've'

$$\therefore \boxed{x = 16}$$

(iii)  $(\sqrt{41})_x = 5_{10}$

Sol:-  $(\sqrt{41})_x = 5$

$$(\sqrt{41})^2 = 5^2$$


$$\therefore (41)_x = 25$$

$$4x^1 + 1x^0 = 25$$

$$4x = 24$$

$$\therefore \boxed{x = 6}$$

## EXOR function :-

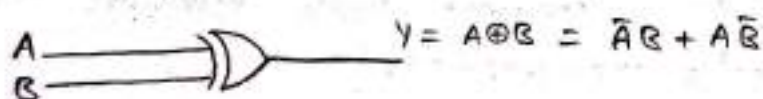

A	B	A ⊕ B
0	0	0
0	1	1
1	0	1
1	1	0

## EXOR Properties :-


1.  $A \oplus A = 0$
2.  $A \oplus \bar{A} = 1$
3.  $A \oplus 1 = \bar{A}$  (Inverter)
4.  $A \oplus 0 = A$  (Non-Inverter)

## Alternative gate representation :-


### 1. NOT Gate :-



### 2. NAND Gate

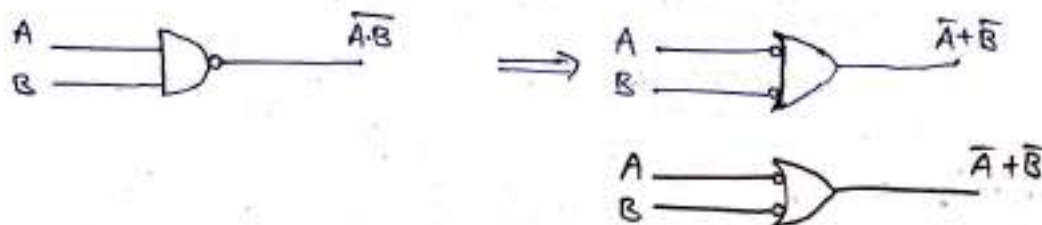

### 3. NOR Gate

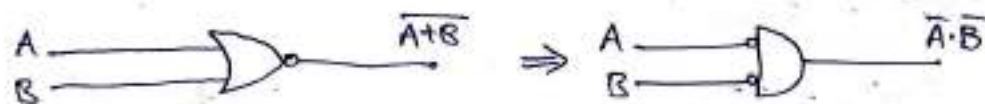


### 4. AND Gate





# 5. OR Gate

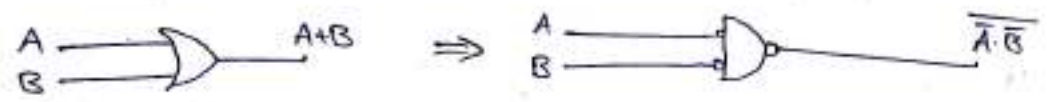

conversion of AND, OR, NOT logic to NAND logic


using Graphical procedure :-

Rules:-

- (i) Draw logic circuit using logic circuit use basic gates.
- (ii) If it is an AND gate place a bubble at output side.
- (iii) If it is an OR gate place a bubble at input side.
- (iv) Place a NOT gate where we placed the bubble.
- (v) Replace bubbled AND by using NAND.
- (vi) Eliminate double inverters.


Ex:-  $Y = AB + A\bar{C}$  using NAND logic.

Sol:- Step 1:- using basic logic gates.

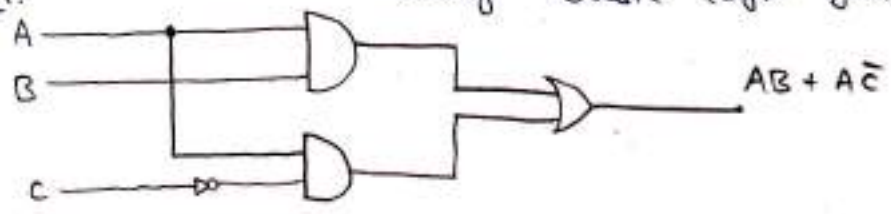



Graphical method.

Step 2:-

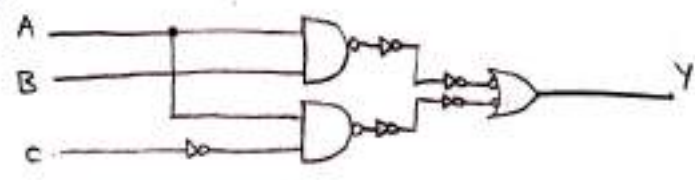


Step 3:-

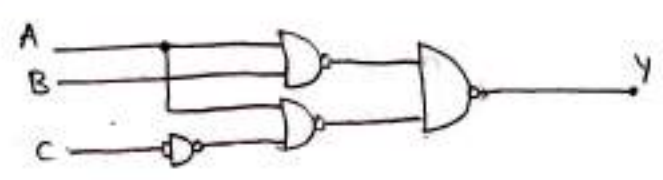

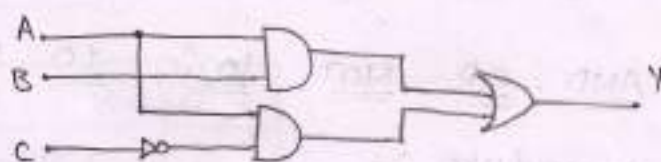Ex:- $Y = AB + A\bar{C}$  using NOR Gate.Sol:-Step 1:-

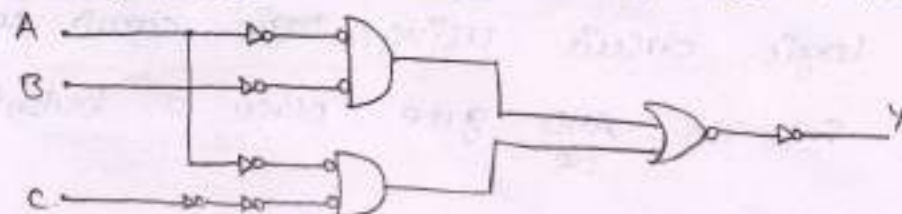Step 2:- In OR gate place a bubble at o/p side & place a NOT gate.  
In AND gate place a bubble at i/p side & place a NOT gate.



Step 3:- Replace bubble AND with by using NOR.

